


## 19 Capacitance

### 19.1 Capacitors and capacitance


Candidates should be able to:

- 1 define capacitance, as applied to both isolated spherical conductors and to parallel plate capacitors
- 2 recall and use  $C = Q/V$
- 3 derive, using  $C = Q/V$ , formulae for the combined capacitance of capacitors in series and in parallel
- 4 use the capacitance formulae for capacitors in series and in parallel

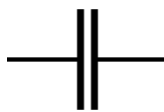- Capacitors are electrical devices used to store energy in electronic circuits.
- The circuit symbol for capacitor is shown below



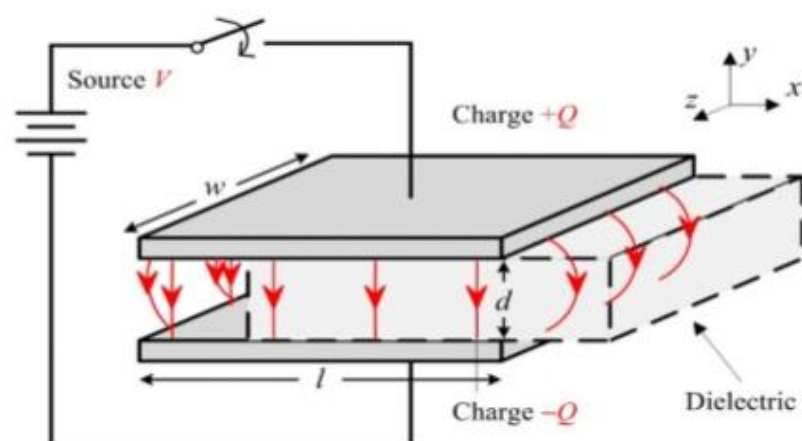- They come in two forms
  - Isolated spherical conductor
  - Parallel plates
- The unit of capacitor is **capacitance**.
- **Capacitance** is defined as **the charge stored per unit potential difference**.
- The higher the capacitance, the greater the energy that can be stored in a capacitor.
- A parallel plate capacitor is made up of two conductive metal plates connected to a voltage supply



- The negative terminal of the voltage supply pushes electrons onto one plate, making it negatively charged.

- The electrons are repelled from the opposite plate, making it positively charged.
- There is commonly a dielectric in between the plates to prevent the charge from free flow between them.
- The capacitance ( $C$ ) of a capacitor is defined by the equation

$$C = \frac{Q}{V}$$

- The SI unit is in **Farad (F)**
- If the capacitor is made of parallel plates,  $Q$  is the charge on the plates and  $V$  is the potential difference across the capacitor.
- For spherical conductor,  $Q$  is the charge stored on its plates.
- The capacitance of a charged sphere is defined by the charge per unit potential at the surface of the sphere.
- Recall that the potential ( $V$ ) of an isolated point charge is given by

$$V = \frac{Q}{4\pi\epsilon_0 r}$$

Substituting into the capacitance equation we get the equation for capacitance ( $C$ ) of a sphere

$$C = 4\pi\epsilon_0 r$$

- For capacitor in **series**, recall that the total voltage ( $V_T$ ) is given by

$$V_T = V_1 + V_2$$

Substituting


$$V = \frac{Q}{C}$$

Into the equation above we get

$$\frac{Q}{C_{total}} = \frac{Q}{C_1} + \frac{Q}{C_2}$$


Since the current is the same for a series circuit, Q will cancel out. If you have more capacitors the equation will become
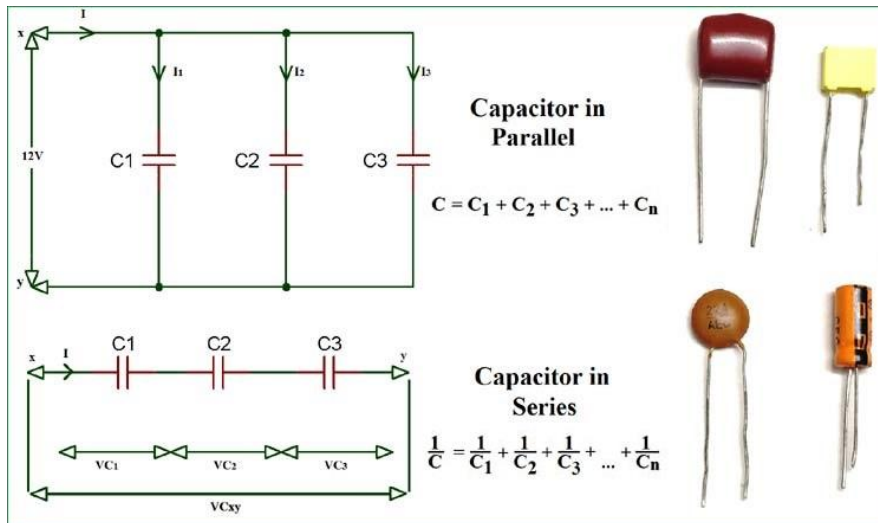
$$\frac{Q}{C_{total}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_2} + \dots$$



- For capacitors in parallel start with

$$Q_T = Q_1 + Q_2$$

 


You should get

$$C_T = C_1 + C_2 + C_3 + \dots$$
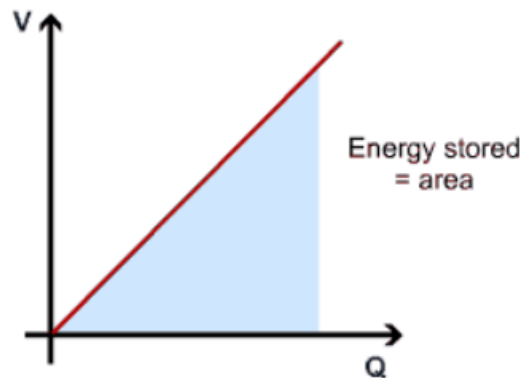
## 19.2 Energy stored in a capacitor

Candidates should be able to:

- 1 determine the electric potential energy stored in a capacitor from the area under the potential–charge graph
- 2 recall and use  $W = \frac{1}{2}QV = \frac{1}{2}CV^2$



- The charge (Q) on a capacitor is **directly proportional** to its potential difference (V).
- The area under the curve of a potential-charge graph is equal to the area under a **triangle**.
- This **area** is the **energy stored** in a capacitor.
- The energy stored (W) is therefore

$$W = \frac{1}{2} QV$$

Substituting  $Q = CV$  we get


$$W = \frac{1}{2} CV^2$$

### 19.3 Discharging a capacitor

Candidates should be able to:

- 1 analyse graphs of the variation with time of potential difference, charge and current for a capacitor discharging through a resistor
- 2 recall and use  $\tau = RC$  for the time constant for a capacitor discharging through a resistor
- 3 use equations of the form  $x = x_0 e^{-(t/RC)}$  where  $x$  could represent current, charge or potential difference for a capacitor discharging through a resistor

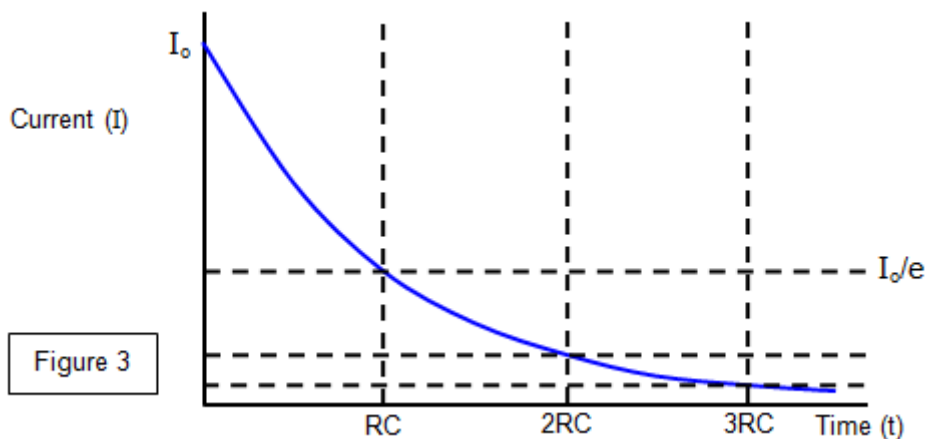- When a capacitor is being charged, the electrons flow from the positive to negative plate.
- When the capacitor is being discharged through a resistor, the electrons flow back from negative plate to the positive plate until there are equal number of electrons on each plate.
- At the start of the discharge, the current is large and gradually falls to zero.



- As a capacitor discharges, the  $I$ ,  $V$  and  $Q$  all decrease exponentially.
- This is represented by an exponential decay in the graph above.
- $V$  and  $Q$  versus time graphs have a similar shape as well.
- The rate at which a capacitor discharges depends on the **resistance** ( $R$ ) of the circuit.
- A **high resistance** will **slow down the discharge** since the current will decrease.
- A **low resistance** will **increase the rate of discharge** since current can flow more freely.
- The time constant of a capacitor discharging through a resistor is a measure of how long it takes for the capacitor to discharge.
- **Time constant ( $\tau$ )** is defined as **the time taken for the charge of a capacitor to decrease to 0.37 of its original value**

$$\tau = RC$$

- The equations below can be used to determine how much current (I), potential difference (V) and charge (Q) left after a certain amount of time from its initial  $I_0$ ,  $V_0$  and  $Q_0$ .

$$I = I_0 e^{-\frac{t}{RC}}$$

$$V = V_0 e^{-\frac{t}{RC}}$$

$$Q = Q_0 e^{-\frac{t}{RC}}$$