

21 Alternating currents


An understanding of the practical and economic advantages of transmission of power by electricity from Cambridge IGCSE / O Level Physics or equivalent is assumed.

21.1 Characteristics of alternating currents

Candidates should be able to:

- 1 understand and use the terms period, frequency and peak value as applied to an alternating current or voltage
- 2 use equations of the form $x = x_0 \sin \omega t$ representing a sinusoidally alternating current or voltage
- 3 recall and use the fact that the mean power in a resistive load is half the maximum power for a sinusoidal alternating current
- 4 distinguish between root-mean-square (r.m.s.) and peak values and recall and use $I_{\text{r.m.s.}} = I_0 / \sqrt{2}$ and $V_{\text{r.m.s.}} = V_0 / \sqrt{2}$ for a sinusoidal alternating current

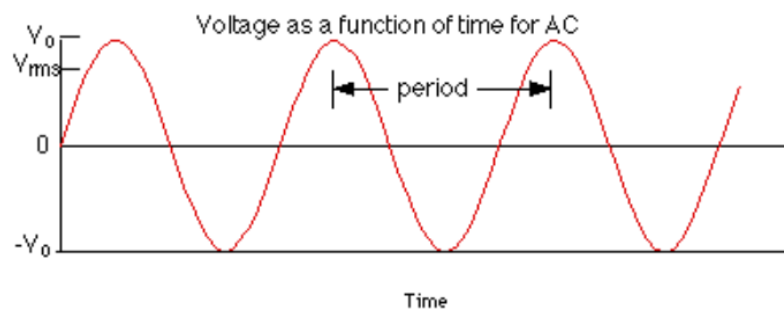- **AC current** is defined as a periodically varying current that changes from positive to negative and has a magnitude that changes with time.



- To find the frequency of an AC current just use

$$T = 1/f$$

- The peak current (I_0) or peak voltage (V_0) is the maximum value of the AC or alternating voltage.
- The equations that can be used to represent AC or voltage are

$$I = I_0 \sin(\omega t)$$

$$V = V_0 \sin(\omega t)$$

- The **rms value** of an AC or voltage is defined as **the value of a constant current/ voltage that produces the same power in a resistor as the alternating current/ voltage.**
- The rms value represent the dc value producing the same heating effect or power dissipation as the AC value.

- RMS can be calculated from

$$I_{rms} = \frac{I_0}{\sqrt{2}}$$

$$V_{rms} = \frac{V_0}{\sqrt{2}}$$

- For mean power (P_{mean}) in AC, the maximum power is related to the I_{rms} by

$$P_{mean} = I_{rms}R$$

Recall that

$$P = I_0^2R$$

Therefore

$$P = 2I_{rms}R = 2P_{mean}$$

$$P_{mean} = P/2$$


- The mean power in a resistive load is only half the max power for AC

21.2 Rectification and smoothing


Candidates should be able to:

- distinguish graphically between half-wave and full-wave rectification
- explain the use of a single diode for the half-wave rectification of an alternating current
- explain the use of four diodes (bridge rectifier) for the full-wave rectification of an alternating current
- analyse the effect of a single capacitor in smoothing, including the effect of the values of capacitance and the load resistance

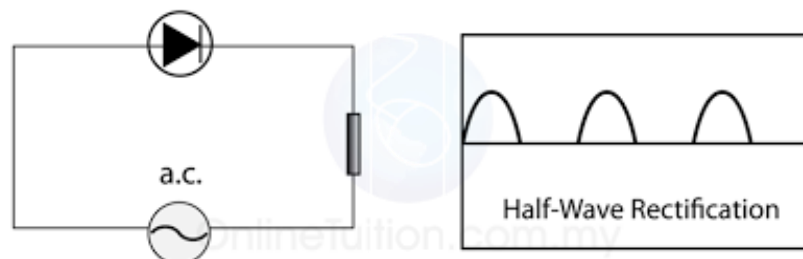
- Rectification is the process of converting AC into DC.**
- There are two types of rectification
 - half-wave rectification**



-full-wave rectification

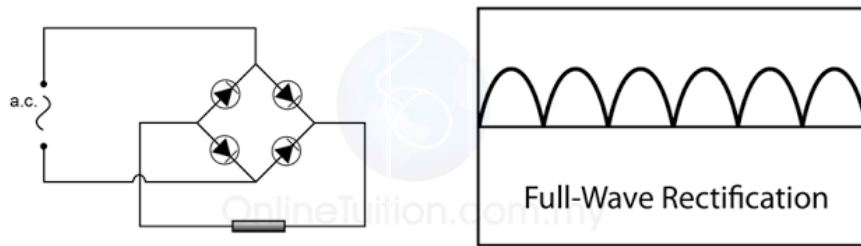

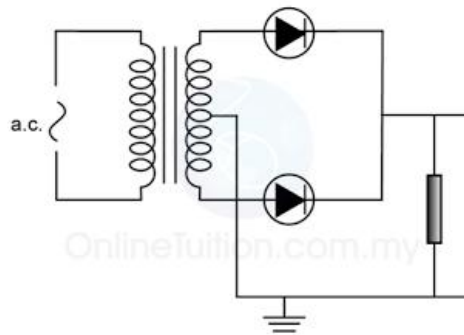- Smoothing can be done with a capacitor to reduce the variation of the output voltage and current.



- A single capacitor is connected in parallel with a load resistor.
- The capacitor is charged from the input voltage and maintains the voltage at a high level.
- When the rectified voltage drops, the capacitor discharges.
- When the voltage rises again the capacitor is charged again.
- The amount of smoothing is controlled by the capacitance (C) of the capacitor and the resistor (R).
- The slower the capacitor discharges, the more smoothing that occurs.
- Recall $\tau = RC$.
- You can increase the discharge time by increasing C or R .
- This means that τ of the capacitor must be greater than the time interval between **adjacent peaks** of the AC or voltage.